

---


# Chapter 7 Flip-Flops and Related Devices

触发器以及相关设备


---

- **Logic circuits**

 - **Combinational Circuits (组合电路)**
- **Sequential Circuits (时序电路)**



**Basic Block**

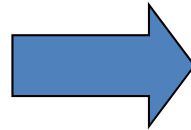

**Flip-Flops**

---

## ● *Objectives*

- Latches (锁存器)
- Edge-triggered Flip-Flops (边沿触发器)
  - S-R FF
  - D FF
  - J-K FF
  - T FF

---

## 7.1 Latches (锁存器)


- The *latch* is a type of temporary device that has two stable states (*bistable*) and is normally placed in a category separate from that of *flip-flops*.
- The difference between latches and flip-flops is the method used for changing their states.

---


## ● *Latches*

- S-R (Set-Reset) Latch (SR锁存器)
- Gated S-R Latch (门控锁存器)
- Gated D (Data) Latch

## 7.1.1 S-R (Set-Reset) Latch



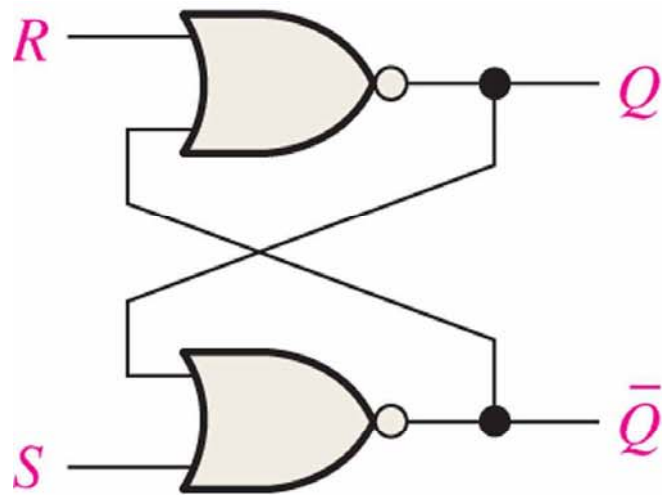


(a) Active-HIGH input S-R latch

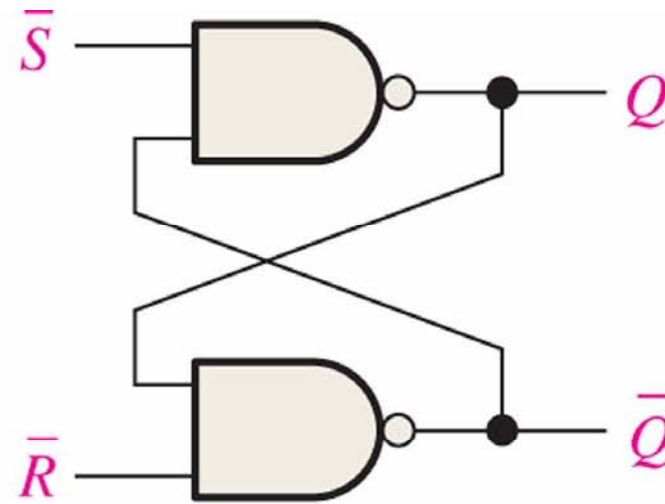


(b) Active-LOW input  $\bar{S}$ - $\bar{R}$  latch


# Active-LOW input S-R latch

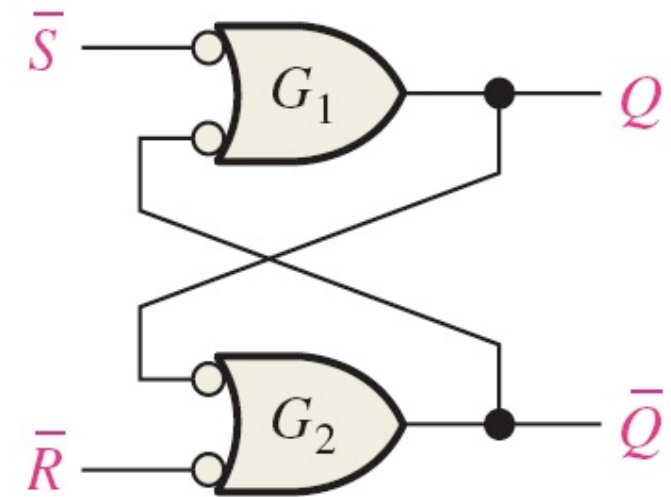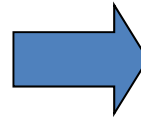 

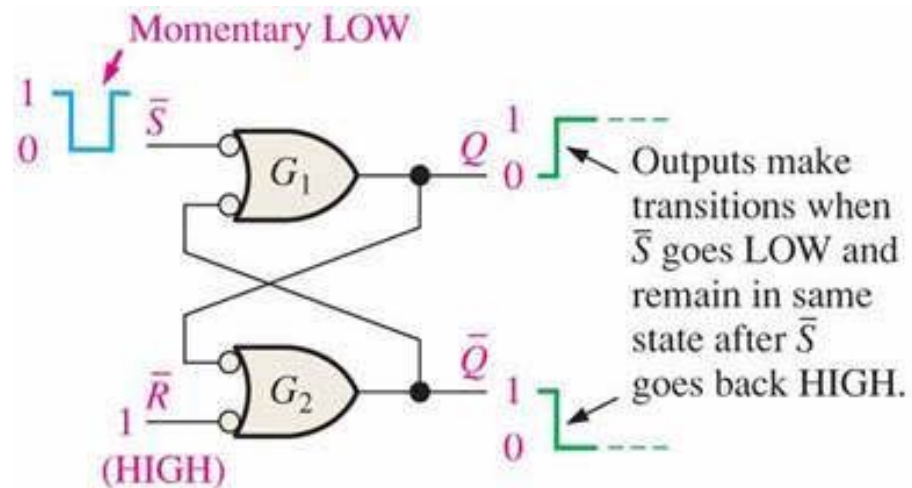(b) Active-LOW input  $\bar{S}$ - $\bar{R}$  latch




Latch starts out RESET ( $Q = 0$ ).

 


Latch starts out SET ( $Q = 1$ ).

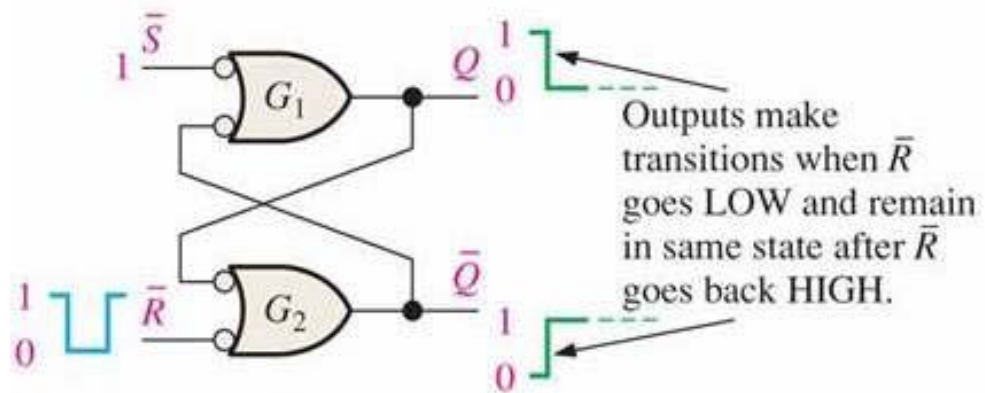(a) Two possibilities for the SET operation






Latch starts out SET ( $Q = 1$ ).

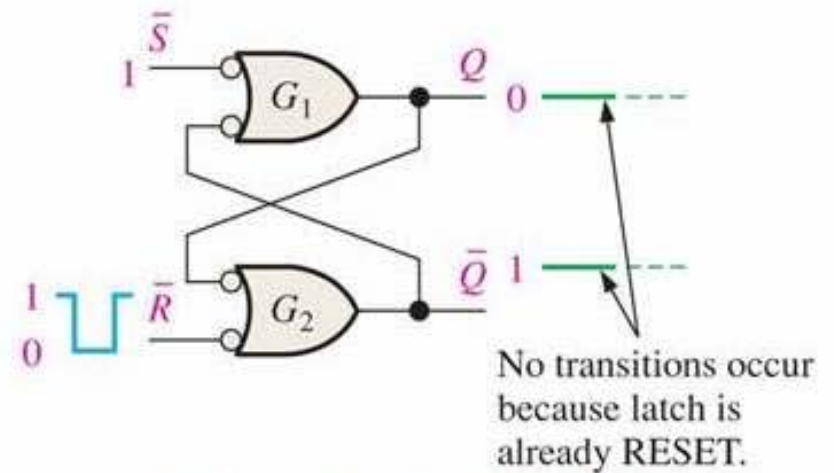


Latch starts out RESET ( $Q = 0$ ).

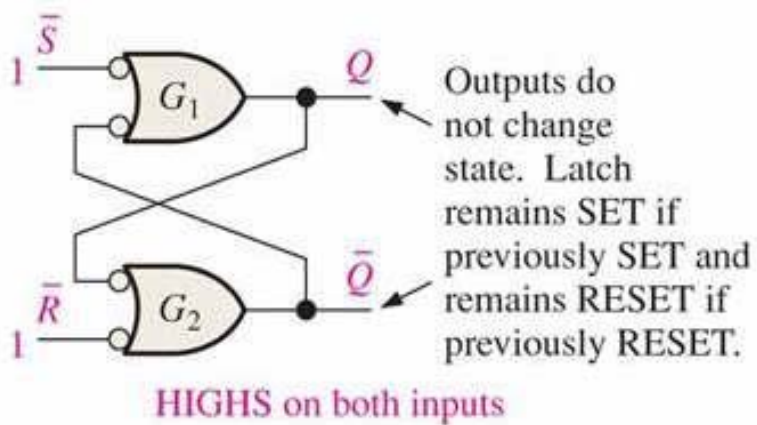(b) Two possibilities for the RESET operation



(c) No-change condition

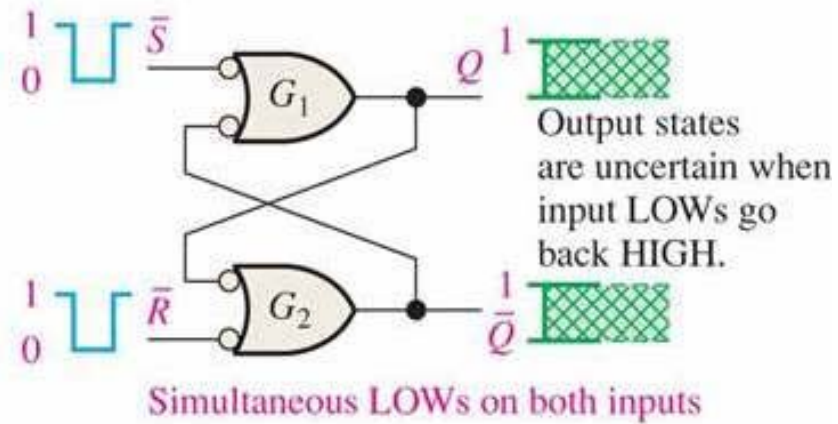


(d) Invalid condition

# Truth Table (真値表)

Inputs		Outputs		Comments
$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$	
1	1	NC	NC	No change. Latch remains in present state.
0	1	1	0	Latch SET.
1	0	0	1	Latch RESET.
0	0	1*	1*	Invalid condition

# Timing diagram

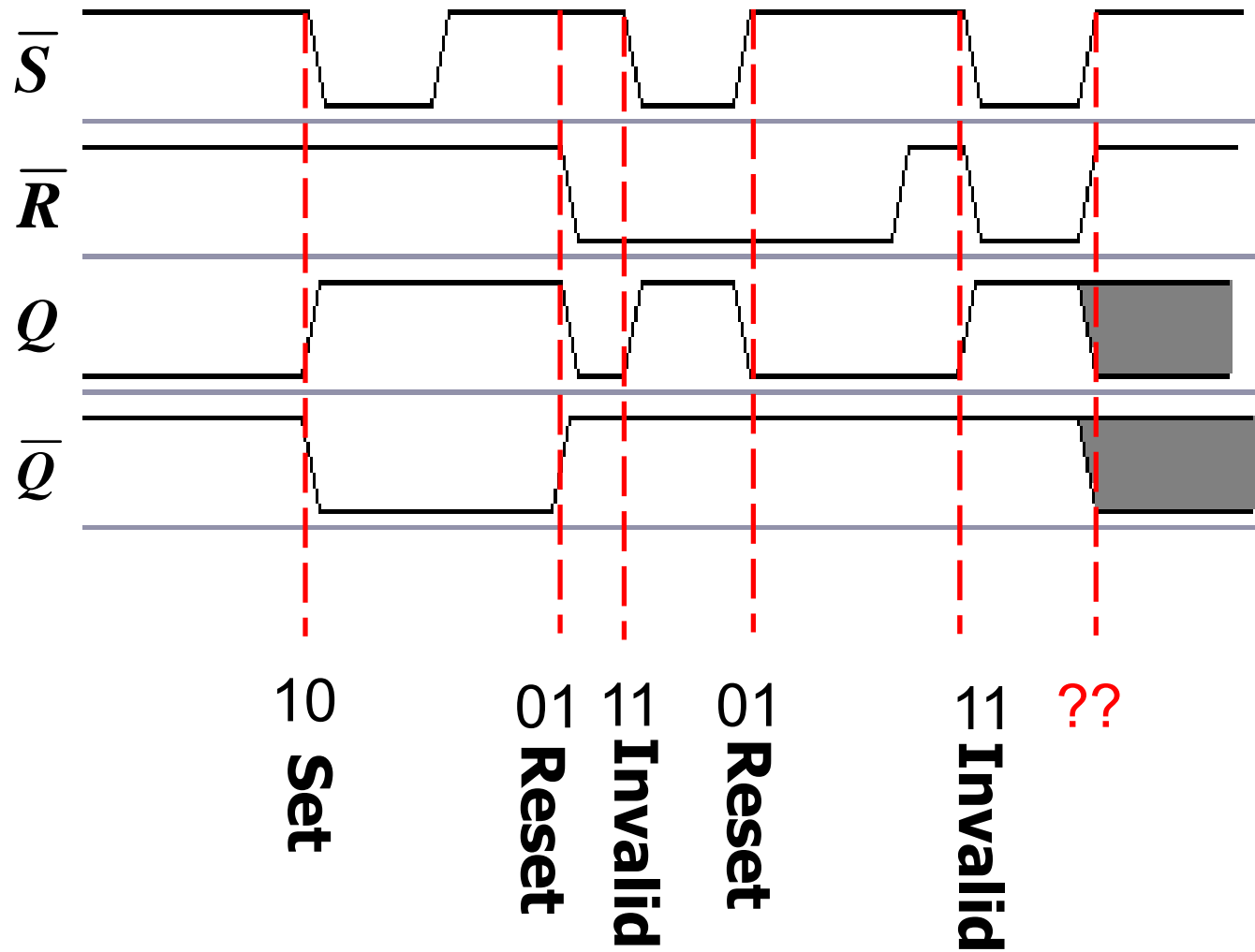


---

# Memory Function


$$\begin{array}{l} S=1; \quad R=0; \left\{ \begin{array}{l} Q=0 \\ \bar{Q}=1 \end{array} \right. \quad \text{“0”, remember “0”} \\ \\ S=0; \quad R=1; \left\{ \begin{array}{l} Q=1 \\ \bar{Q}=0 \end{array} \right. \quad \text{“1”, remember “1”} \end{array}$$

**Bi-stable**

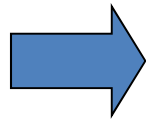


**Used to store 1 bit  
binary number**

# Active-HIGH input S-R latch

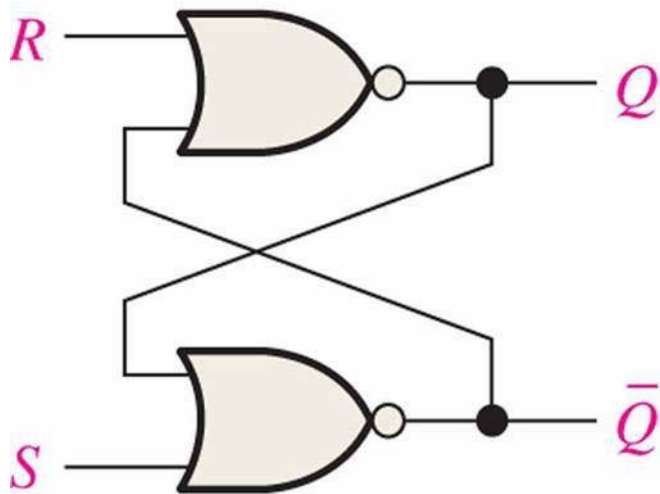


R	S	Q	$\bar{Q}$
0	0	$Q_0$	$\bar{Q}_0$
0	1	1	0
1	0	0	1
1	1	0*	0*

# Logic Symbol

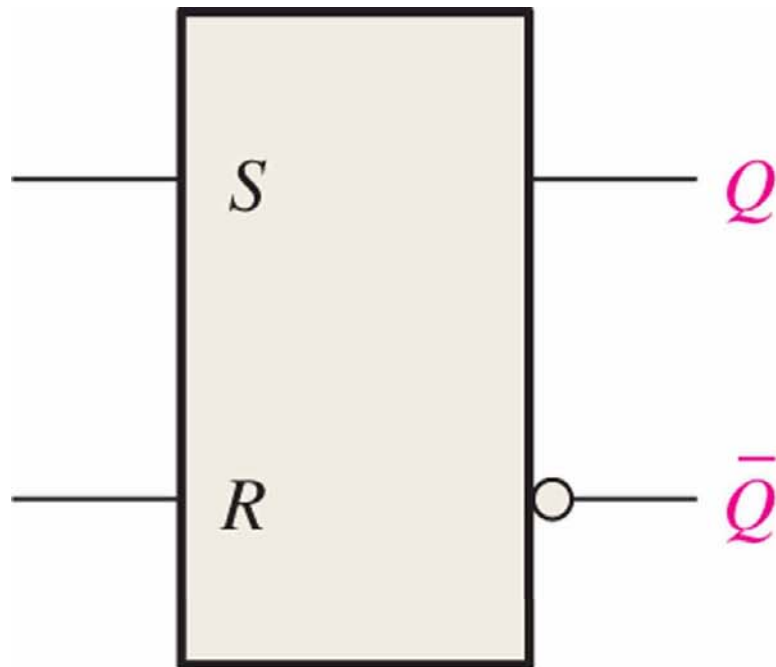


(a) Active-HIGH input  
S-R latch

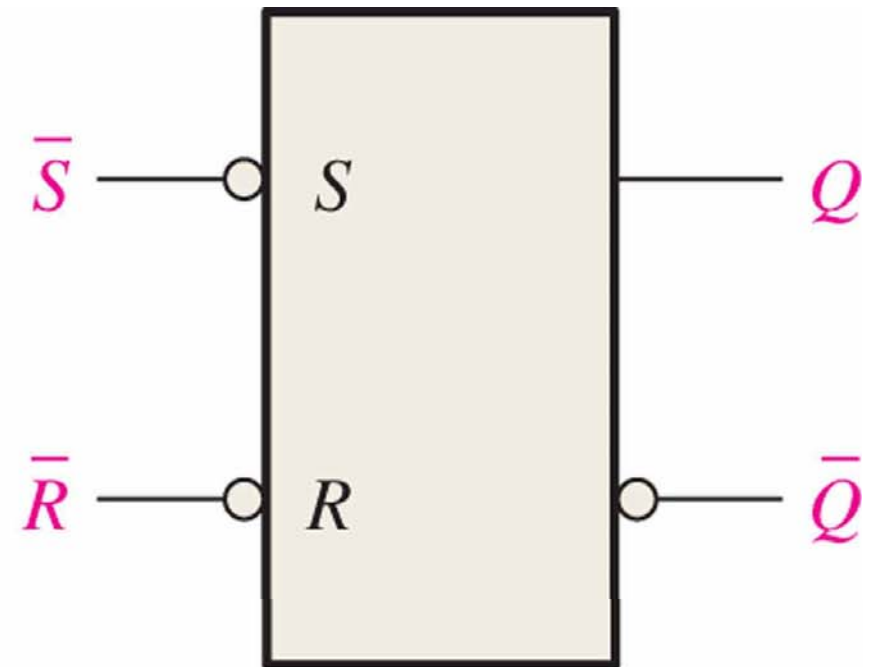


(b) Active-LOW input  
 $\bar{S}$ - $\bar{R}$  latch

# Application Example

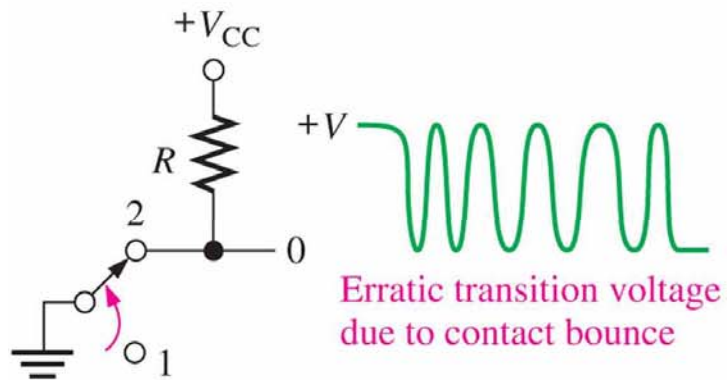


(a) Switch contact bounce

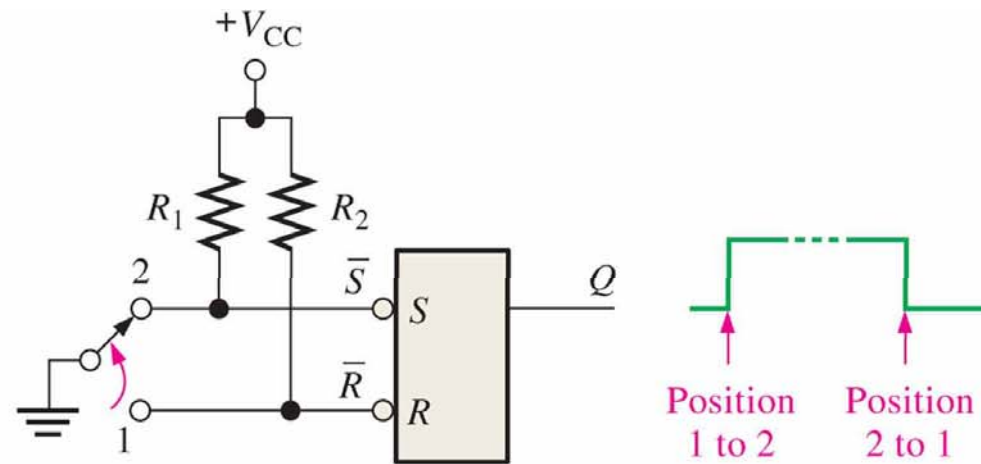


(b) Contact-bounce eliminator circuit



# 74LS279

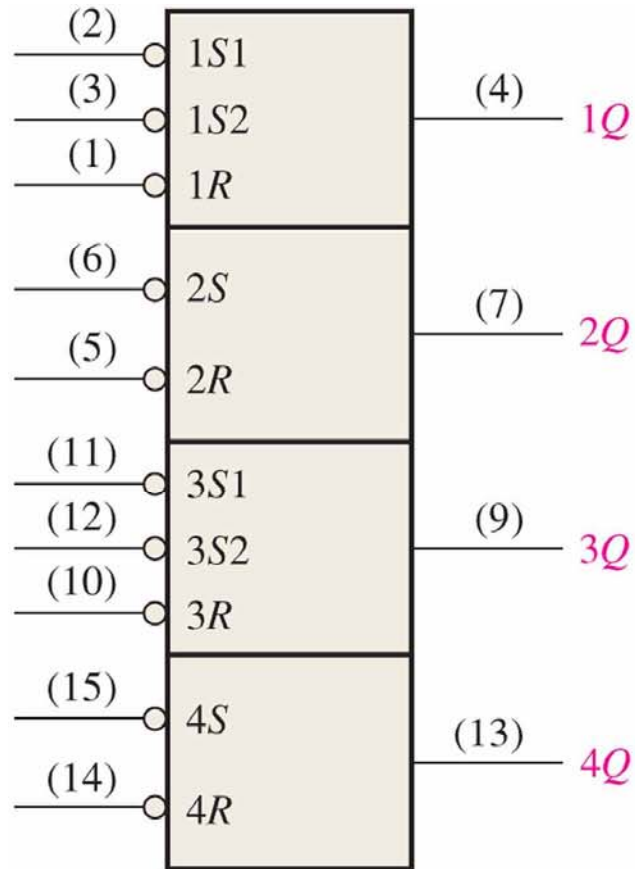


(a) Logic diagram

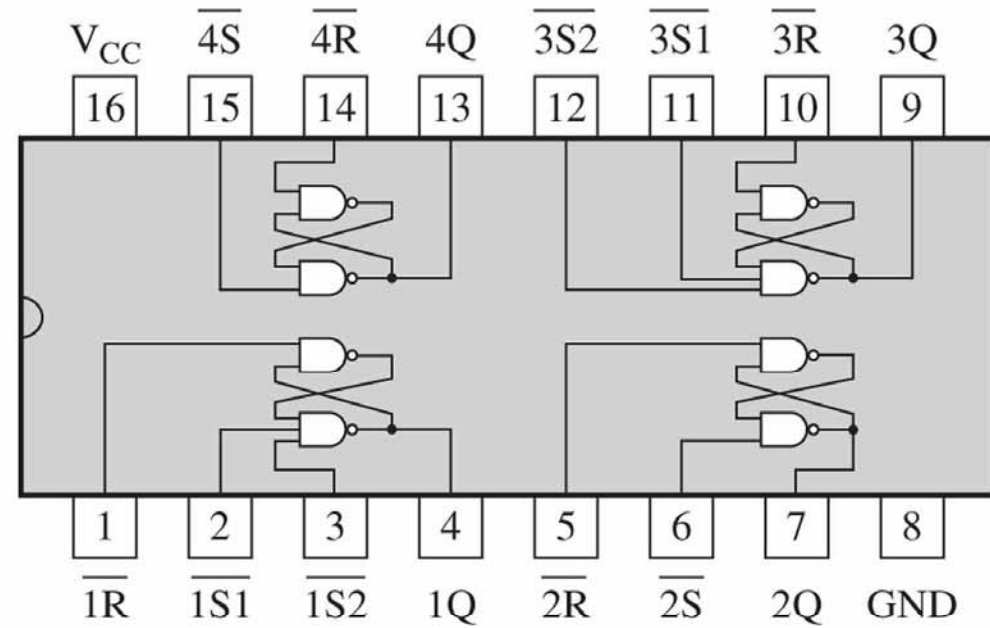


(b) Pin diagram
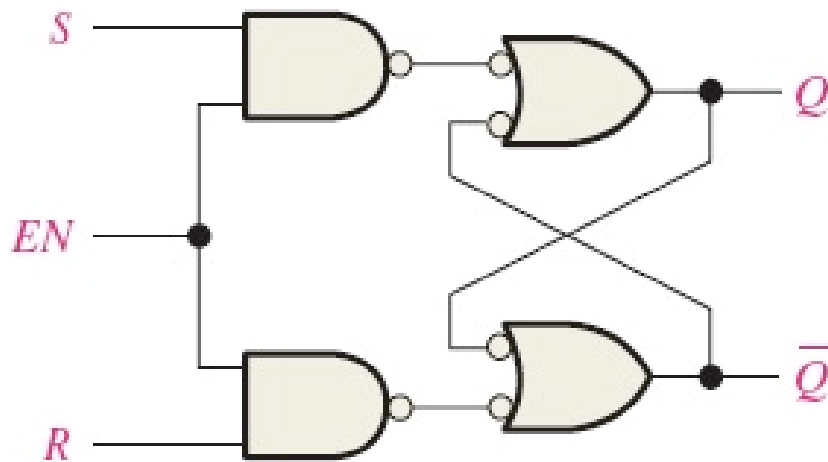
## 7.1.2 The Gated S-R Latch (门控S-R锁存器)

**EN:** control the time when the inputs S and R can control the output. (Level-triggered)





(a) Logic diagram

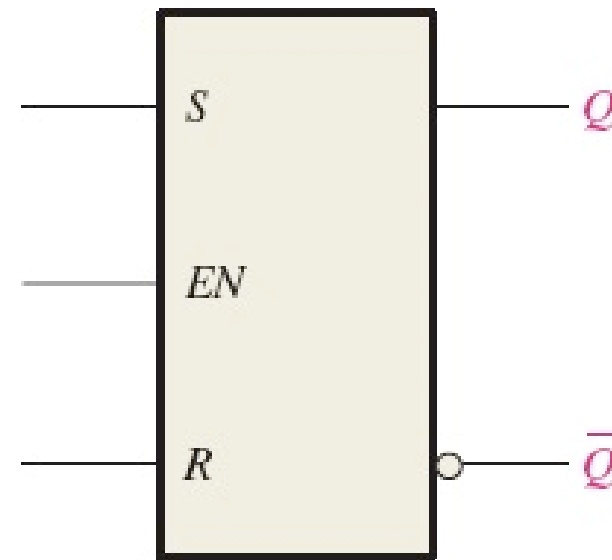


(b) Logic symbol

# Comparison

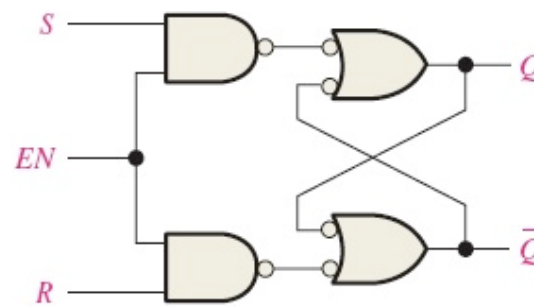 

(a) Logic diagram

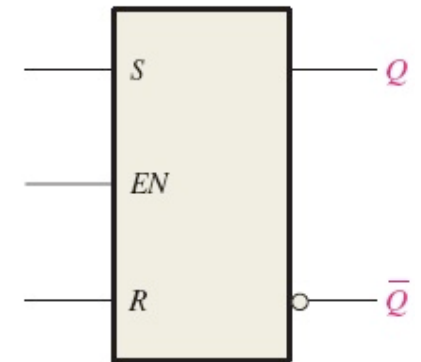


(b) Logic symbol


R	S	Q	$\bar{Q}$
0	0	$Q_0$	$\bar{Q}_0$
0	1	1	0
1	0	0	1
1	1	$1^*$	$1^*$

E	R	S	Q	$\bar{Q}$
0	X	X	$Q_0$	$\bar{Q}_0$
1	0	0	$Q_0$	$\bar{Q}_0$
1	0	1	1	0
1	1	0	0	1
1	1	1	$1^*$	$1^*$


# Gated S-R Latch Waveform

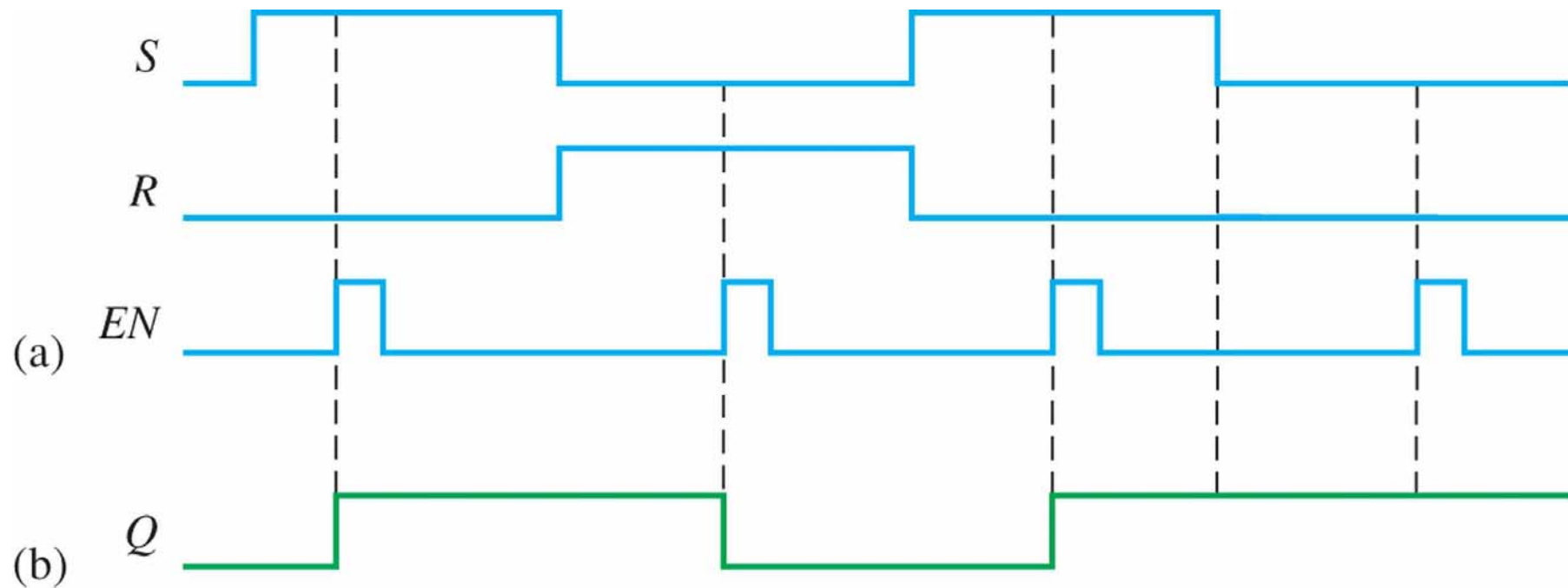


## 7.1.3 The Gated D Latch

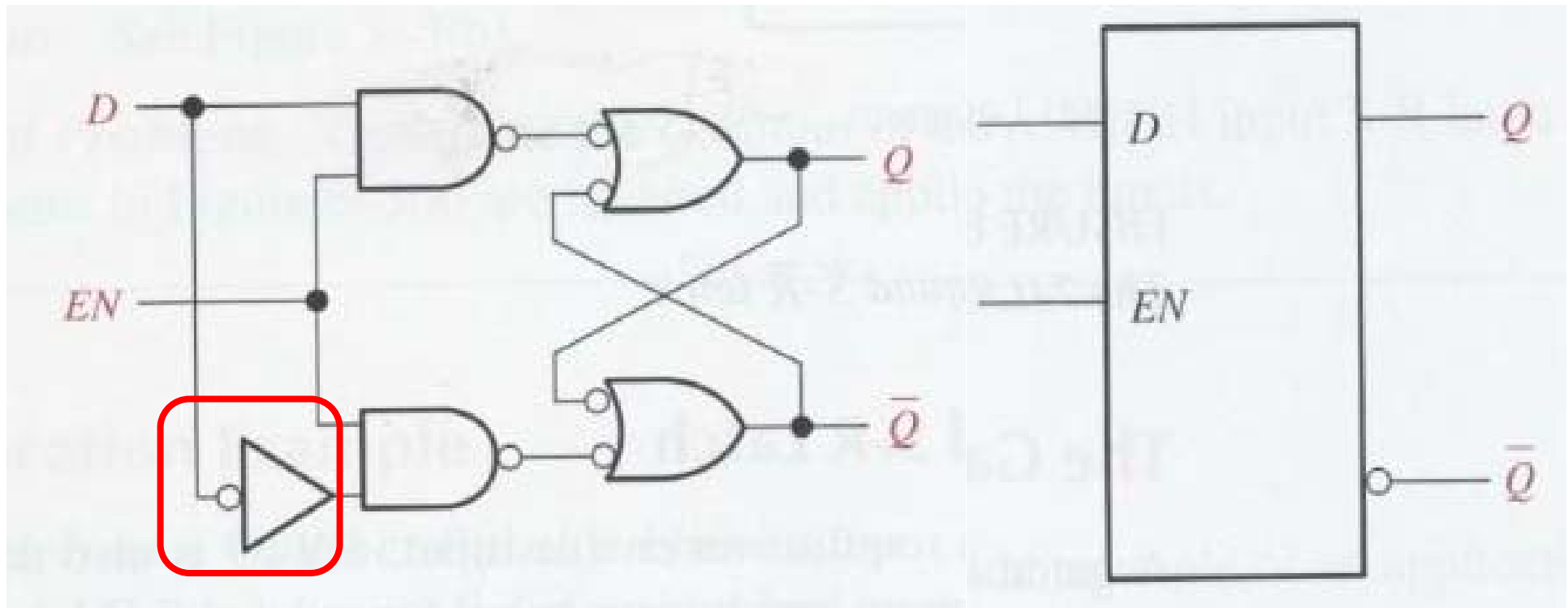

# Gated D Latch Waveform

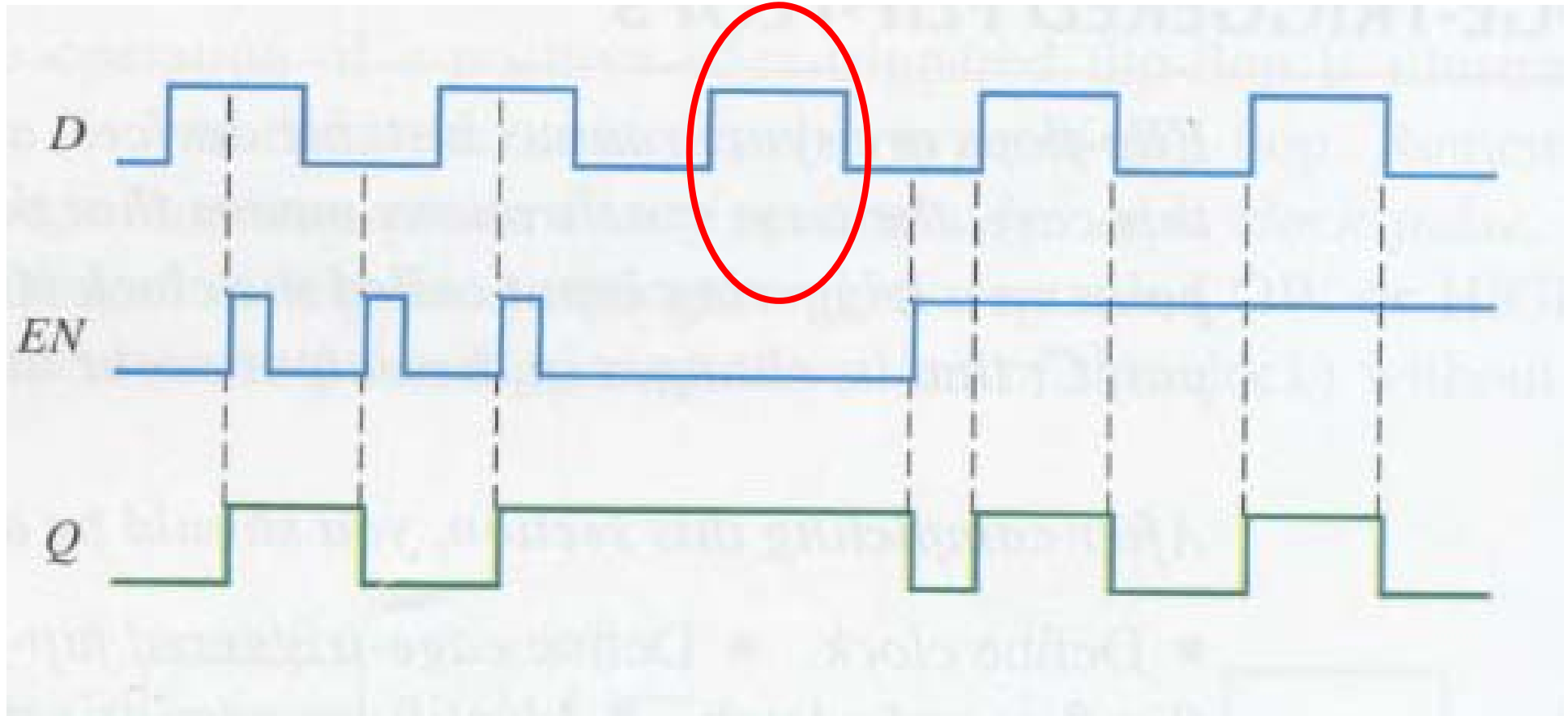

# 74LS75

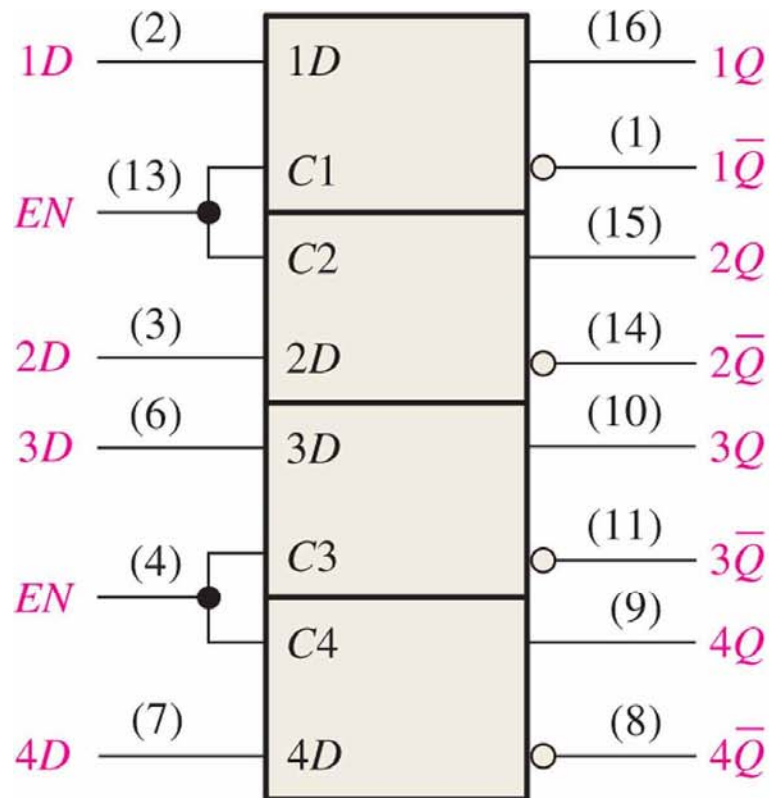

(a) Logic symbol

INPUTS		OUTPUTS		COMMENTS
$D$	$EN$	$Q$	$\bar{Q}$	
0	1	0	1	RESET
1	1	1	0	SET
X	0	$Q_0$	$\bar{Q}_0$	No change

Note:  $Q_0$  is the prior output level before the indicated input conditions were established.

(b) Truth table (each latch)

# Application example: Latches for temporary data storage

